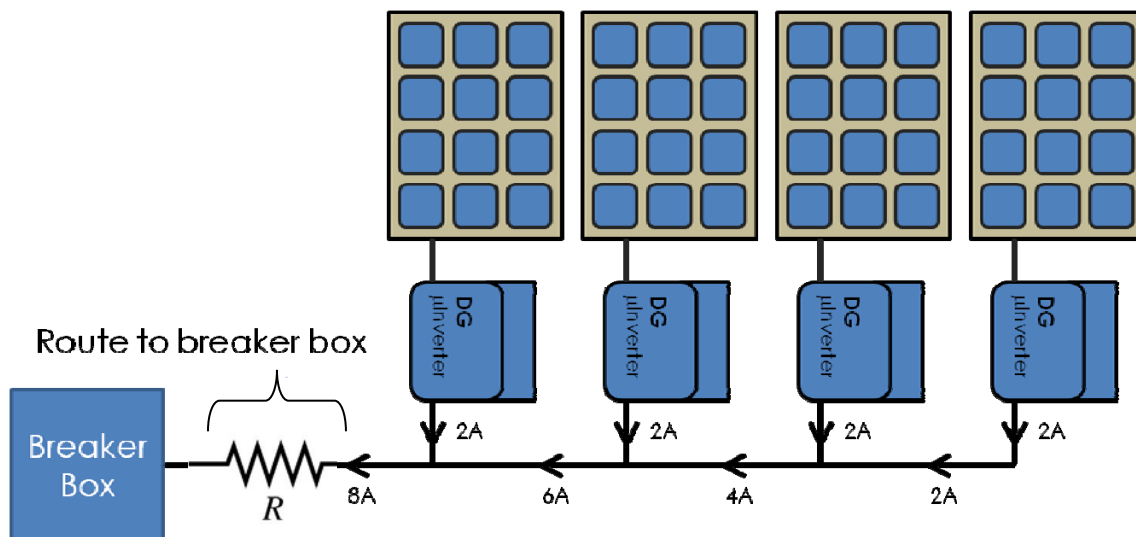


# MICRO INVERTERS VOLTAGE RISE CALCULATIONS

## Line Voltage Rise

When micro inverters are strung together on an (end fed) AC branch, each segment carries more current as you get closer to the breaker.

Voltage (V)= Current (I) x Resistance (R)···each segment of the AC branch has a finite resistance R. As a result, there is a voltage rise from the breaker to the last inverter on the branch.




## MICRO INVERTERS VOLTAGE RISE CALCULATIONS (cont.)
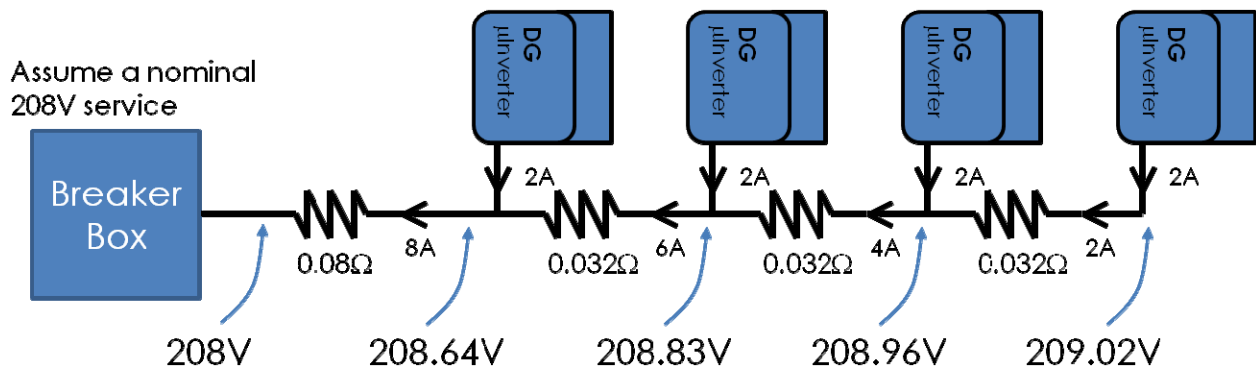
### Example of Voltage Rise Calculation

Assume the Following:

- Micro inverters are placed 4 meters apart.
- The common route from the breaker to the first inverter (trunk route) is 10 meters long.
- Each micro inverter can provide a max of 2A.



Why are all these resistances double 0.004 /m\*length?

Answer: Because there are 2 lines to an AC connection, each with a resistance.

## MICRO INVERTERS VOLTAGE RISE CALCULATIONS (cont.)

### Why Should You Care About Voltage Rise?

- Per UL and VDE standards inverters have to shut off if the line voltage exceeds 10%
- For a 208V service, this would be around 228V above nominal.
- Assuming it could be within reason for the service at your site to run 5% high to start with. In such a scenario, there is only a 5% budget left for voltage rise (about 10V)
- Our previous example with only 4 inverters with 10AWG AC branch was well below 10V, but lets consider a larger AC branch with 16 inverters (below)

### Example with 16 inverters in “end fed” AC Branch

General Formula for Rise in AC Branch:

$$V_{rise} = N * I_{max} * R_{trunk} + \left( \frac{N^2 + N}{2} - 1 \right) * I_{max} * R_{inv2inv}$$


For this Example:  $I_{max} = 2A$ ,  $R_{trunk} = 0.08\Omega$ ,  $R_{inv2inv} = 0.032\Omega$ ,  $N = 16$

$$V_{rise} = 16 * 2 * 0.08 + \left( \frac{256 + 16}{2} - 1 \right) * 2 * 0.032 = 11.2V$$

At 11.2V, 16 four meter spaced inverters “end fed” with 10AWG would be an issue.

## MICRO INVERTERS VOLTAGE RISE CALCULATIONS (cont.)

### Center Fed AC Branch

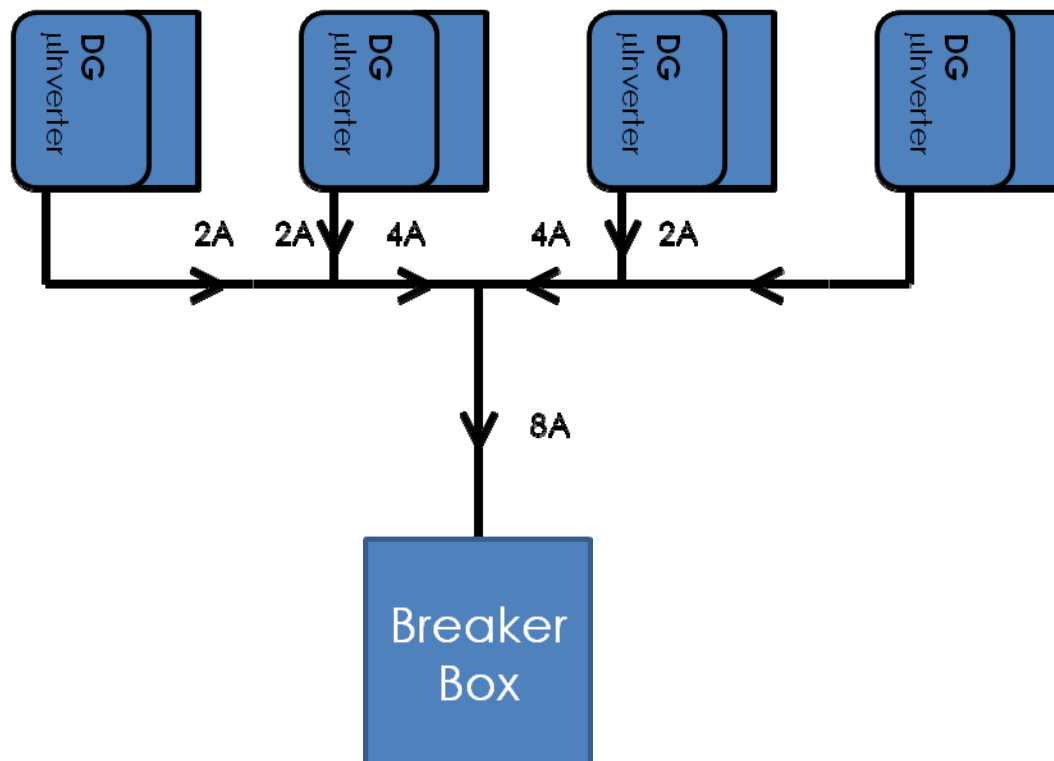

- With a “center fed” AC Branch, both the currents and distances along the branch are cut in half. Therefore  $V_{rise}$  along the trunk is cut to  $\frac{1}{4}$ .
- The trunk feed from the Breaker Box to the AC branch remains the same.



## MICRO INVERTERS VOLTAGE RISE CALCULATIONS (cont.)

### Vrise Formula with “Center Fed” AC Branch

For Center Fed AC Branches the Following Applies:

$$V_{rise} = N * I_{max} * R_{trunk} + \left( \frac{N^2}{8} + \frac{N}{4} - 0.5 \right) * I_{max} * R_{inv2inv}$$

For our same example:  $N=16$ ,  $R_{trunk}=0.08\Omega$ ,  $R_{inv2inv}=.032\Omega$ ,  $I_{max}=2A$

$$V_{rise} = 16 * 2 * 0.08 + \left( \frac{256}{8} + \frac{16}{4} - 0.5 \right) * 2 * .032 = 4.832V$$

**Conclusion:** Paying attention to Voltage rise across the AC connection is important to ensure all inverters remain on and producing power. When possible, use a center fed AC branch topology to mitigate voltage rise in the AC connection.